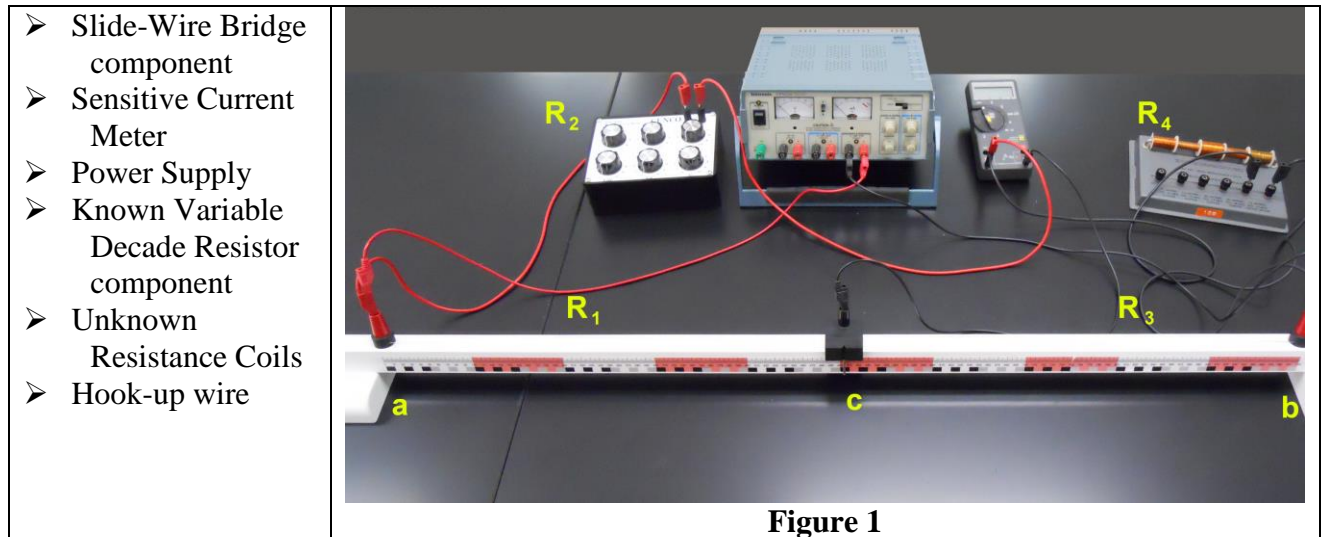


E12a: Resistance & the Slide-Wire Wheatstone Bridge

Introduction:

The Wheatstone Bridge, named after Charles Wheatstone, is a circuit that is designed to make very precise measurements of resistance. The basic design of the bridge circuit is so effective that it has also been included in other types of precision measurement components such as transducers and strain gauges. This experiment makes use of a Slide-Wire Wheatstone Bridge, explained more in the **Discussion** section, to explore the relationships between the resistance of a conductor and the properties of the conductor such as its length and resistivity. In the slide-wire bridge the resistance can be transposed from two known resistors to two known lengths of wire. The ratio of the lengths can then be used to experimentally determine the resistance of an unknown. This experimental resistance is then compared to the theoretical resistance of the unknown, which can be calculated using known properties of the resistor material.

Apparatus:



Discussion:

The bridge circuit is a design that can be constructed with a variety of circuit components depending upon the intended function of the circuit. This specific bridge circuit will be composed of resistors exclusively and will function to measure very small resistances. The basic design for a bridge circuit of resistors is demonstrated in Figure #2.

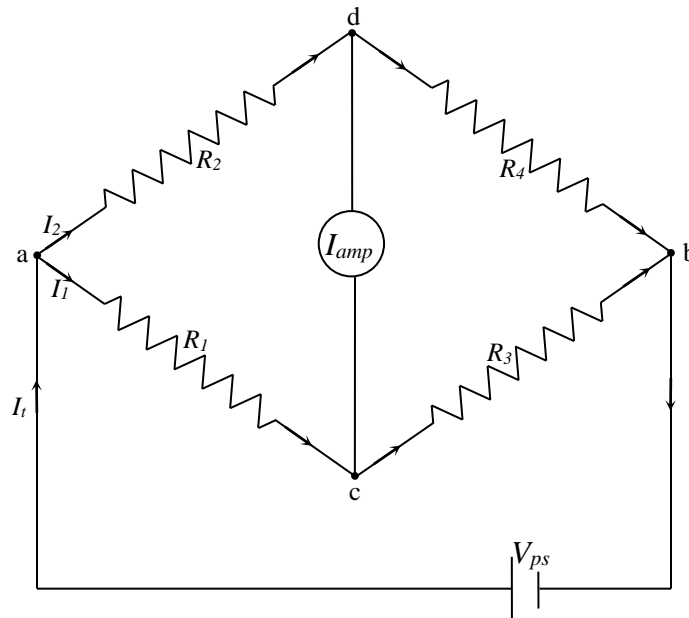


Figure 2

A balanced condition of the bridge exists when no current flows through the meter measuring current (I_{amp}). Applying Kirchhoff's current junction rule and voltage loop rule results in the following expressions.

$$I_t - I_1 - I_2 = 0$$

$$I_1 R_1 - I_2 R_2 = 0$$

$$I_1 R_3 - I_2 R_4 = 0$$

Solving the two voltage equations for a ratio of currents and then combining them develops an expression relating the resistors.

$$\frac{R_2}{R_1} = \frac{R_4}{R_3}$$

This experiment will use the bridge design to measure the resistance of several small unknown resistors. The unknown resistors will be inserted into the resistor R_4 position.

$$R_4 = R_2 \frac{R_3}{R_1}$$

In the slide-wire form of the Wheatstone Bridge resistors R_1 & R_3 are replaced by a length of uniform wire between points (a & b). A sliding contact at point (c) provides a variable resistance ratio between R_1 and R_3 . The resistance of a uniform wire conductor depends on the material, the length and the cross sectional area. This relationship is expressed in the following equation.

$$R = \rho \frac{\text{length}}{\text{area}}$$

In this equation the area is the cross sectional area of the wire and ρ is the resistivity of the wire material. Since the apparatus uses a uniform wire the cross-sectional area and the resistivity are constant for the length of the wire. This makes the ratio of resistance equivalent to the ratio of length.

$$R_4 = R_2 \left(\frac{\rho l_{cb} / \text{area}}{\rho l_{ac} / \text{area}} \right)$$

$$R_4 = R_2 \frac{l_{cb}}{l_{ac}}$$

This last equation is used to experimentally determine the resistance of each of the unknown resistors.

The unknown resistors for the experiment are coils of wire. The wire coils will have varying lengths, diameters and materials. The theoretical resistance of a conductor depends on the material, the length, the cross sectional area and the temperature. The relationship is the same as express above for a uniform wire conductor.

$$R_{theo} = \rho \frac{\text{Length}}{\text{Area}}$$

In this equation Area is the cross sectional area of the conductor, Length is the total length of the conductor from connection junction to connection junction and ρ is the resistivity of the material. Resistivity is a property of the material from which the conductor is made and is also dependent upon the temperature of the conductor. Table I provides the specifics for the coils used in the experiment. This information along with the above equation is used to calculate the theoretical resistance for each of the unknown resistors. Note: in Table I the resistivities are given for a temperature of 20 degrees Celsius.

Table I

Coil #	Material	Resistivity <i>(ohm cm) 20°C</i>	Diameter <i>(cm)</i>	Length <i>(cm)</i>
1	copper	1.678×10^{-6}	.0644	1000
2	copper	1.678×10^{-6}	.0311	1000
3	copper	1.678×10^{-6}	.0644	2000
4	copper	1.678×10^{-6}	.0311	2000
5	nickel silver	28.8×10^{-6}	.0644	1000

Procedures:

1. Analyze the set-up of the apparatus shown in **Figure 1**.
2. Calculate the theoretical resistance value for each unknown resistor (coil of wire) (Refer to experiment E4 to calculate the series and parallel resistor values). Check with a lab instructor in order to verify the theoretical resistances before proceeding.
3. Connect the first unknown resistance to the slide-wire bridge in the R_4 position.
4. Select an appropriate value for the known resistance on the decade resistor. This selected value should be similar to the resistor calculated in step 2.
5. Move the contact point (c) along the slide-wire until the position where the current meter indicates zero is found.
6. Measure l_{ac} & l_{cb} and calculate the experimental unknown resistance.
7. Compare the theoretical and experimental resistance values. If they are not similar check the bridge connections. Also examine if a different known resistor permits a better experimental determination. Any extra trial done to look for a better experimental value of the resistance should be documented in the data sheet.
8. Repeat the process using the other unknown resistors.

Experiment E12a: Resistance & the Slide-Wire Wheatstone Bridge

Student Name _____

Lab Partner Name _____

Lab Partner Name _____

Physics Course _____

Physics Professor _____

Experiment Start Date _____

<i>Lab Assistant Name</i>	<i>Date</i>	<i>Time In</i>	<i>Time Out</i>

Experiment Stamped Completed

Data Sheets: E12a: Resistance & the Slide-Wire Wheatstone Bridge

NAME: _____

DATE: _____

coil #	theoretical resistance R ohms	known resistor R_2 ohms	length ac cm	length cb cm	experimental resistance R_4 ohms
1					
2					
3					
4					
5					
series 1 thru 5					
parallel 4 & 5					

Extra Trials (if needed)

coil #	theoretical resistance R ohms	known resistor R_2 ohms	length ac cm	length cb cm	experimental resistance R_4 ohms