


Name: _____ Date: _____ Course: _____ Professor: _____

E4b Prelab: Simple D.C. Circuits



Read Lab instructions and Watch Videos Before Answering Questions

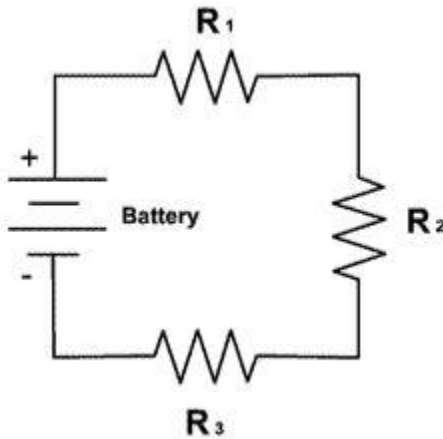1. Vashti has arranged three resistors and a battery into a circuit as shown below. The battery has a voltage of $V = 61 \text{ V}$ and the resistors have resistances of $R_1 = 63 \Omega$, $R_2 = 127 \Omega$, and $R_3 = 867 \Omega$.




- a) Calculate the equivalent resistant of the series circuit.

Hint: Read section 20.6 from your textbook for series wiring (Physics, Cutnell and Johnson).

- b) Using Ohms Law, calculate the total current that Vashti measures.

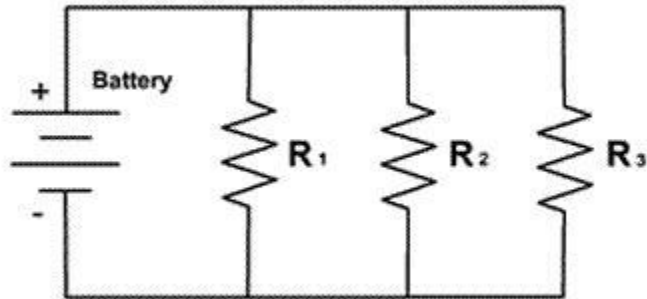2. Vashti rearranges the resistors as shown below ($R_1 = 63 \Omega$, $R_2 = 127 \Omega$, and $R_3 = 867 \Omega$). He keep the same voltage for the Battery ($V = 61 \text{ V}$).



- a) Calculate the equivalent resistance of the parallel circuit.

Hint: Read section 20.7 from your textbook for series wiring (Physics, Cutnell and Johnson).

- b) Using Ohms Law, calculate the total current that they measure.