


Name: \_\_\_\_\_ Date: \_\_\_\_\_ Course: \_\_\_\_\_ Professor: \_\_\_\_\_

## E4b Prelab: Simple D.C. Circuits



Read Lab instructions and Watch Videos Before Answering Questions

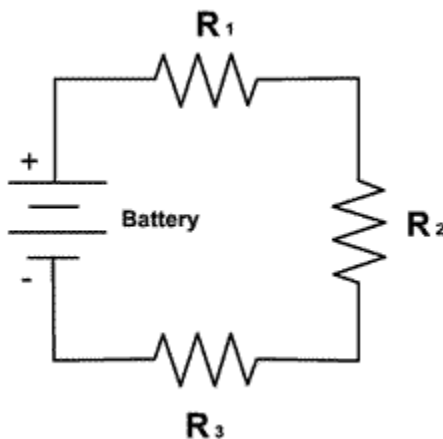1. Vashti has arranged three resistors and a battery into a circuit as shown below. The battery has a voltage of  $V = 52 \text{ V}$  and the resistors have resistances of  $R_1 = 72 \Omega$ ,  $R_2 = 117 \Omega$ , and  $R_3 = 938 \Omega$ .




- a) Calculate the equivalent resistant of the series circuit.

Hint: Read section 20.6 from your textbook for series wiring (Physics, Cutnell and Johnson).

- b) Using Ohms Law, calculate the total current  $I_t$  that Vashti measures.

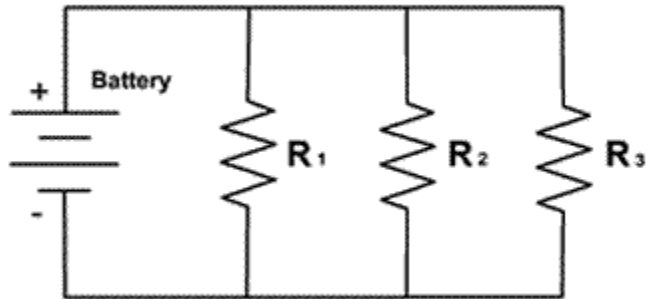2. Vashti rearranges the resistors as shown below ( $R_1 = 72 \Omega$ ,  $R_2 = 117 \Omega$ , and  $R_3 = 938 \Omega$ ). He keep the same voltage for the Battery ( $V = 52 \text{ V}$ ).



- a) Calculate the equivalent resistant of the parallel circuit.

Hint: Read section 20.7 from your textbook for series wiring (Physics, Cutnell and Johnson).

- b) Using Ohms Law, calculate the total current  $I_t$  that they measure.